

Lecture 10  
AC CIRCUITS  
CHAPTER 36

PHYSICS 270

Dennis Papadopoulos

March 1, 2011


# Chapter 36. AC Circuits

## Topics:

- AC Sources and Phasors
- Capacitor Circuits (Capacitive Reactance)
- *RC* Filter Circuits
- Inductor Circuits (Inductive Reactance)
- The Series *RLC* Circuit

## 10.4 Generators

One of the most important applications of Faraday's law of induction is to generators and motors. A generator converts mechanical energy into electric energy, while a motor converts electrical energy into mechanical energy.

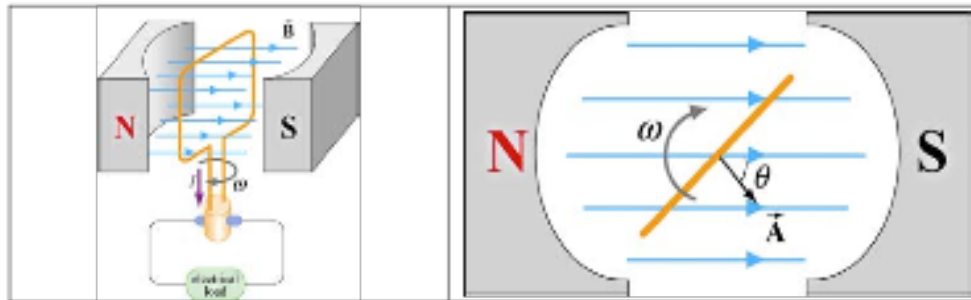

**Figure 10.4.1** (a) A simple generator. (b) The rotating loop as seen from above.

Figure 10.4.1(a) is a simple illustration of a generator. It consists of an  $N$ -turn loop rotating in a magnetic field which is assumed to be uniform. The magnetic flux varies with time, thereby inducing an emf. From Figure 10.4.1(b), we see that the magnetic flux through the loop may be written as



$$\Phi_B = \vec{\mathbf{B}} \cdot \vec{\mathbf{A}} = BA \cos \theta = BA \cos \omega t \quad (10.4.1)$$

The rate of change of magnetic flux is

Creates a emf whose amplitude oscillates with time at frequency  $\omega$

Edison (GE) DC voltage and current – battery. Tesla (Westinghouse) AC ( Alternating) voltage and current. The war of currents won by AC due to step-up step down potential.


**FIGURE 36.1** An oscillating emf can be represented as a graph or as a phasor diagram.

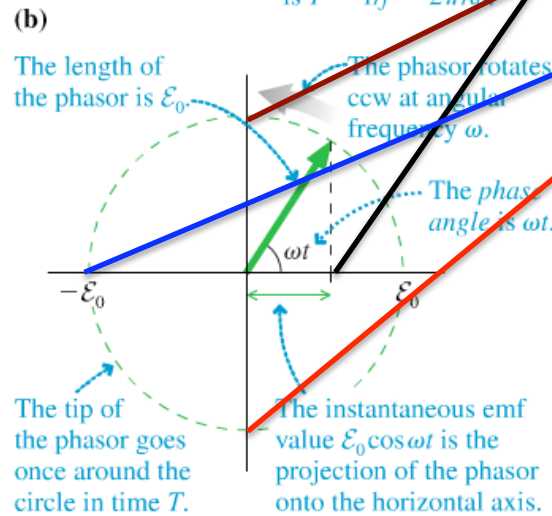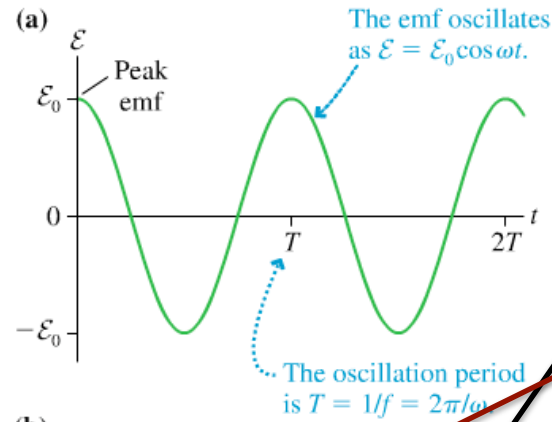

The tip of the phasor goes once around the circle in time  $T$ .

$\text{Cos}(\omega t)$

**FIGURE 36.2** The correspondence between a phasor and points on a graph.

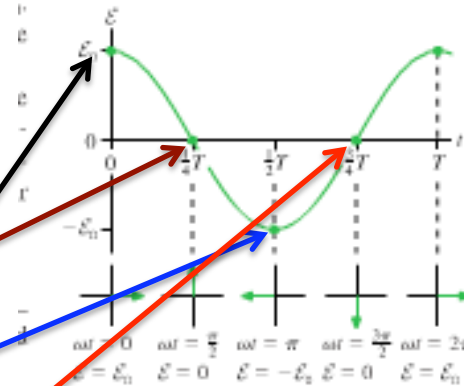


- Phasor is a rotating vector whose:
- 1.Length corresponds to amplitude
  2. Rotates ccw with angular velocity  $\omega$ .
  3. Projection on horizontal (for cos) or vertical (for sin) gives the instantaneous value of the alternating quantity at time  $t$ .

$V(t) = V_0 \sin(\omega t)$


Notes: (1) As the phasor (red vector) rotates, the projection (pink vector) oscillates

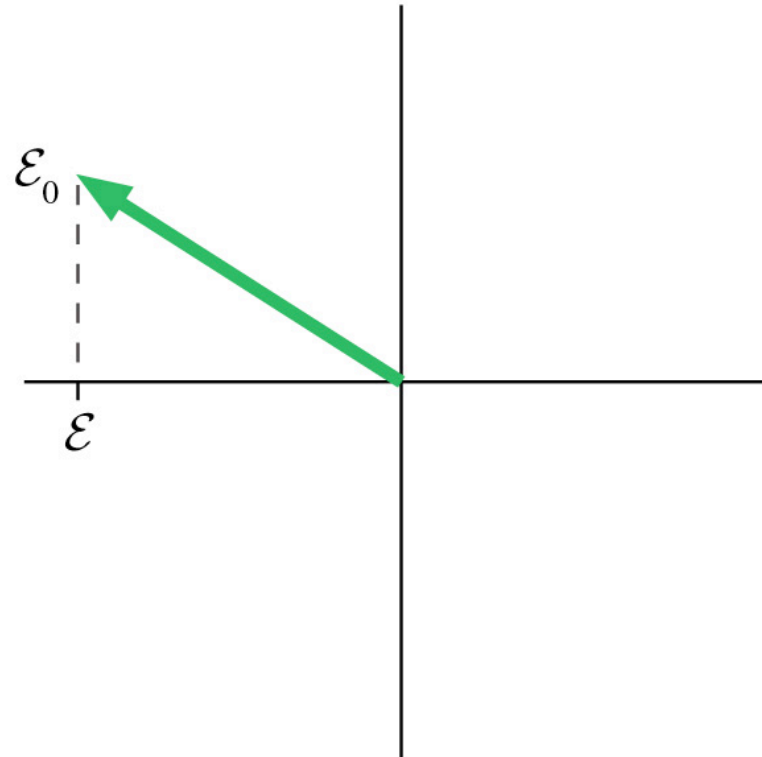The magnitude of the instantaneous value of the emf represented by this phasor is



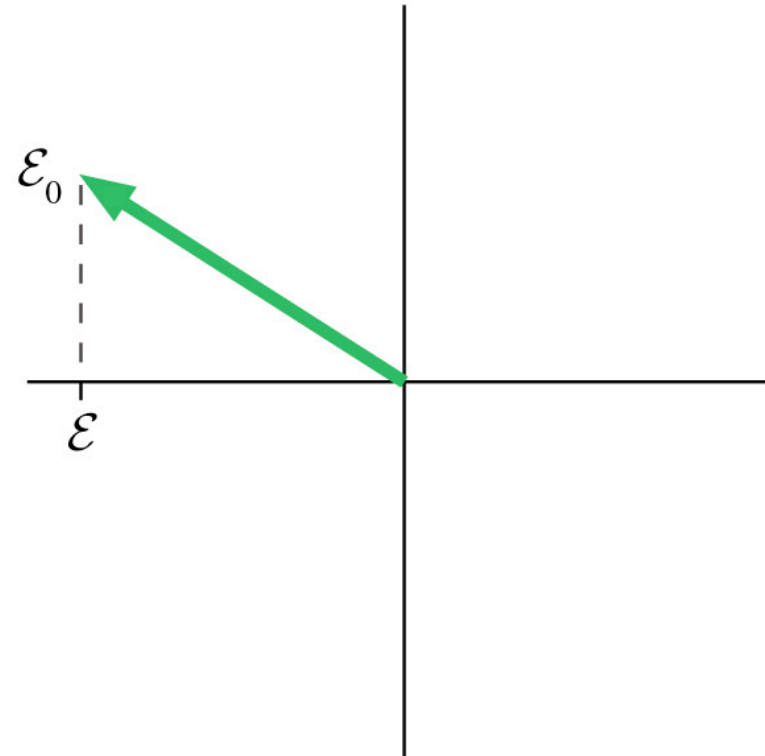
- A. constant.
- B. increasing.
- C. decreasing.
- D. It's not possible to tell without knowing  $t$ .
- E. Other

The magnitude of the instantaneous value of the emf represented by this phasor is




- A. constant.
- B. increasing. (for cos)**
- C. decreasing.(for sin)
- D. It's not possible to tell without knowing  $t$ .

**FIGURE 36.3** Instantaneous current  $i_R$  through a resistor.

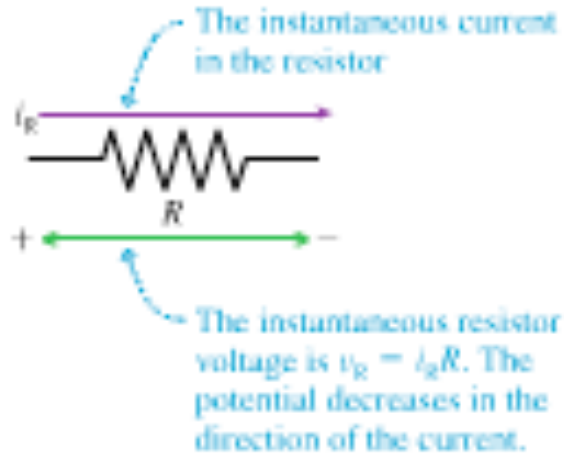


**FIGURE 36.4** An AC resistor circuit.

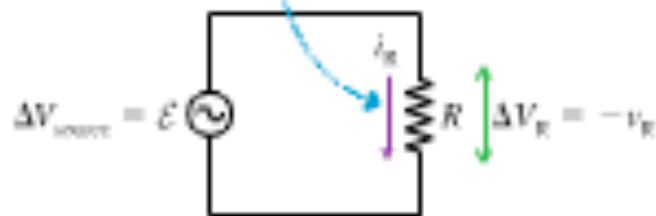This is the current direction when  $\mathcal{E} > 0$ . A half cycle later it will be in the opposite direction.




## AC Resistor circuit

**FIGURE 36.5** Graph and phasor diagram of the resistor current and voltage. The current and voltage are in phase.

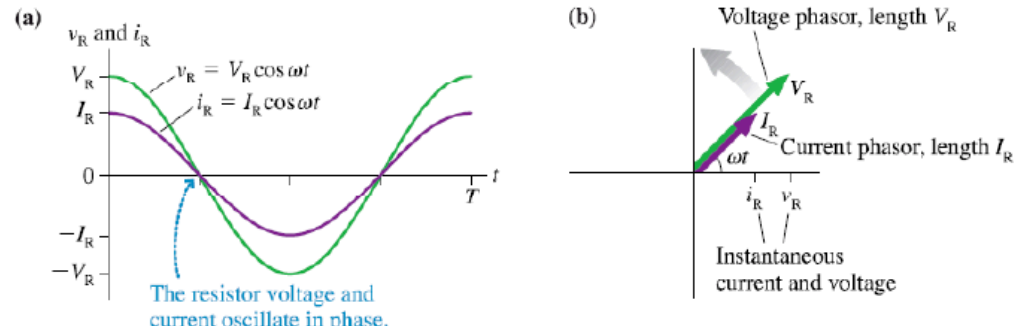


## Cos input

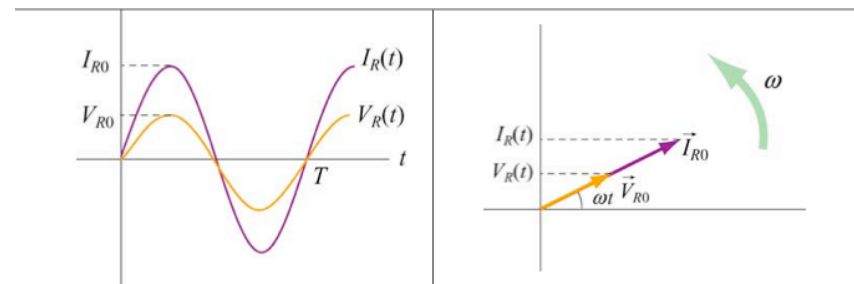

## Sin input


# AC Circuit: Resistors

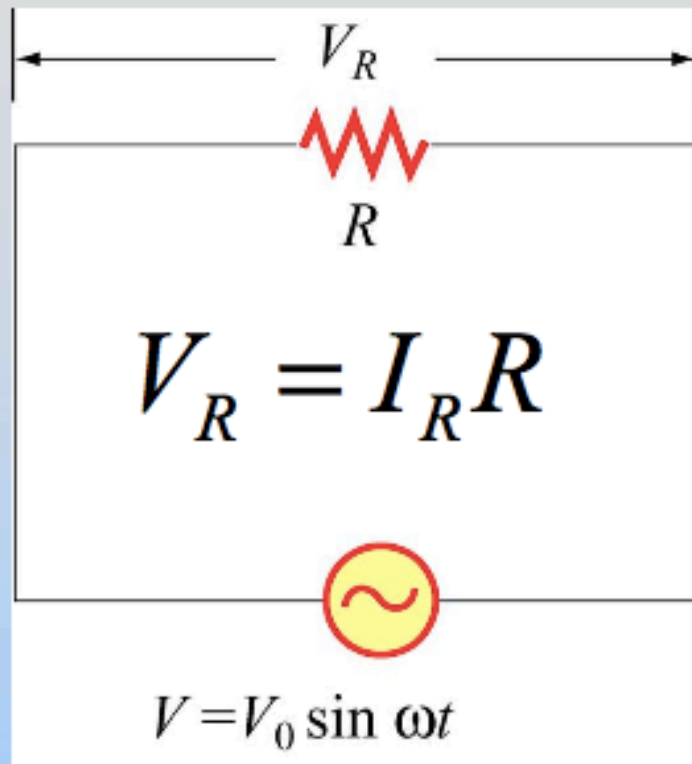

$$I_R = \frac{V_R}{R} = \frac{V_0}{R} \sin \omega t$$
$$= I_0 \sin (\omega t - 0)$$

$$I_0 = \frac{V_0}{R}$$
$$\varphi = 0$$

$I_R$  and  $V_R$  are in phase

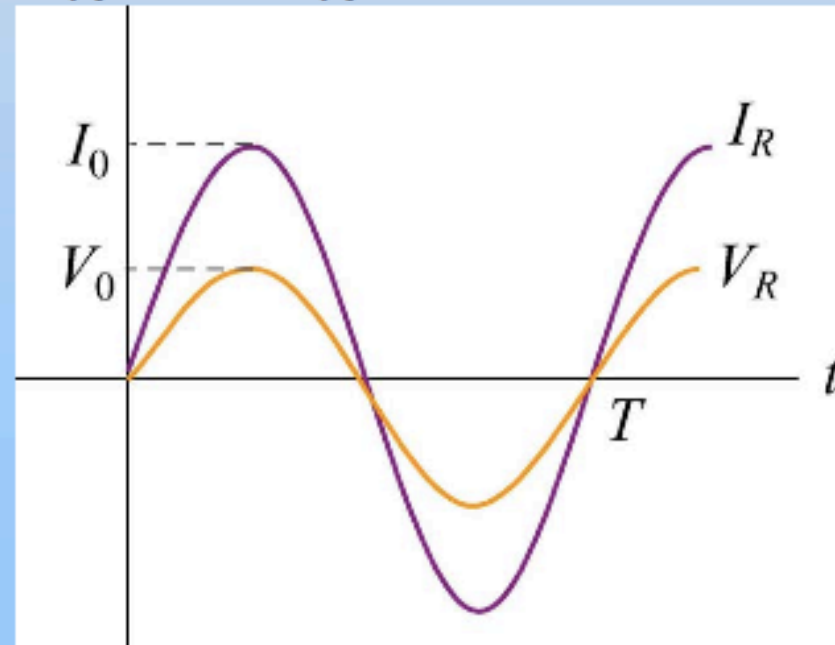




The average value of current over one period can be obtained as:

$$\langle I_R(t) \rangle = \frac{1}{T} \int_0^T I_R(t) dt = \frac{1}{T} \int_0^T I_{R0} \sin \omega t dt = \frac{I_{R0}}{T} \int_0^T \sin \frac{2\pi t}{T} dt = 0 \quad (12.2.3)$$

This average vanishes because

$$\langle \sin \omega t \rangle = \frac{1}{T} \int_0^T \sin \omega t dt = 0 \quad (12.2.4)$$

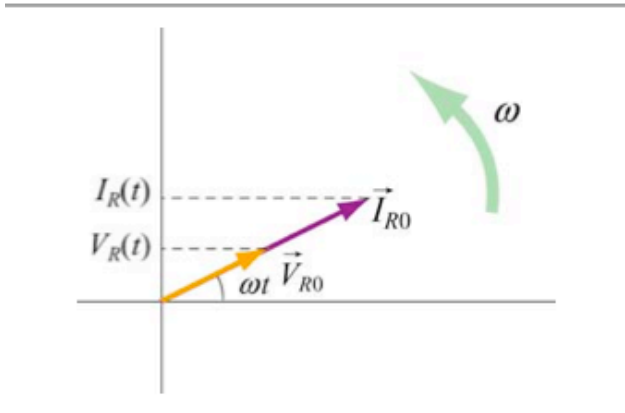Similarly, one may find the following relations useful when averaging over one period:



$$\langle \cos \omega t \rangle = \frac{1}{T} \int_0^T \cos \omega t dt = 0$$

$$\langle \sin \omega t \cos \omega t \rangle = \frac{1}{T} \int_0^T \sin \omega t \cos \omega t dt = 0$$

$$\langle \sin^2 \omega t \rangle = \frac{1}{T} \int_0^T \sin^2 \omega t dt = \frac{1}{T} \int_0^T \sin^2 \left( \frac{2\pi t}{T} \right) dt = \frac{1}{2}$$

$$\langle \cos^2 \omega t \rangle = \frac{1}{T} \int_0^T \cos^2 \omega t dt = \frac{1}{T} \int_0^T \cos^2 \left( \frac{2\pi t}{T} \right) dt = \frac{1}{2}$$

Whether we take sin or cos is a matter of choice. Result the same.  $\langle \sin \rangle = 0$ ,  $\langle \sin^2 \rangle = 1/2$

From the above, we see that the average of the square of the current is non-vanishing:

$$\langle I_R^2(t) \rangle = \frac{1}{T} \int_0^T I_R^2(t) dt = \frac{1}{2} I_{R0}^2$$

It is convenient to define the root-mean-square (rms) current as

$$I_{\text{rms}} = \sqrt{\langle I_R^2(t) \rangle} = \frac{I_{R0}}{\sqrt{2}} \quad (12.2.7)$$

In a similar manner, the rms voltage can be defined as

$$V_{\text{rms}} = \sqrt{\langle V_R^2(t) \rangle} = \frac{V_{R0}}{\sqrt{2}} \quad (12.2.8)$$


The rms voltage supplied to the domestic wall outlets in the United States is  $V_{\text{rms}} = 120$  V at a frequency  $f = 60$  Hz .

The power dissipated in the resistor is


$$P_R(t) = I_R(t) V_R(t) = I_R^2(t) R \quad (12.2.9)$$

from which the average over one period is obtained as:

$$\langle P_R(t) \rangle = \langle I_R^2(t) R \rangle = \frac{1}{2} I_{R0}^2 R = I_{\text{rms}}^2 R = I_{\text{rms}} V_{\text{rms}} = \frac{V_{\text{rms}}^2}{R} \quad (12.2.10)$$

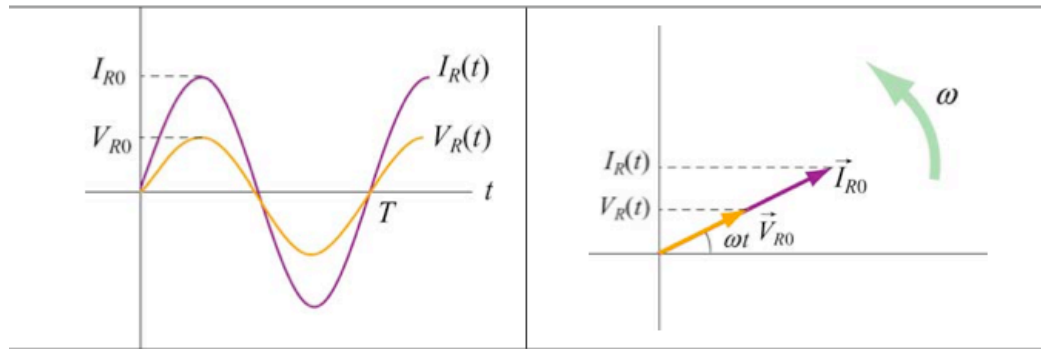

**FIGURE 36.7** An AC capacitor circuit.

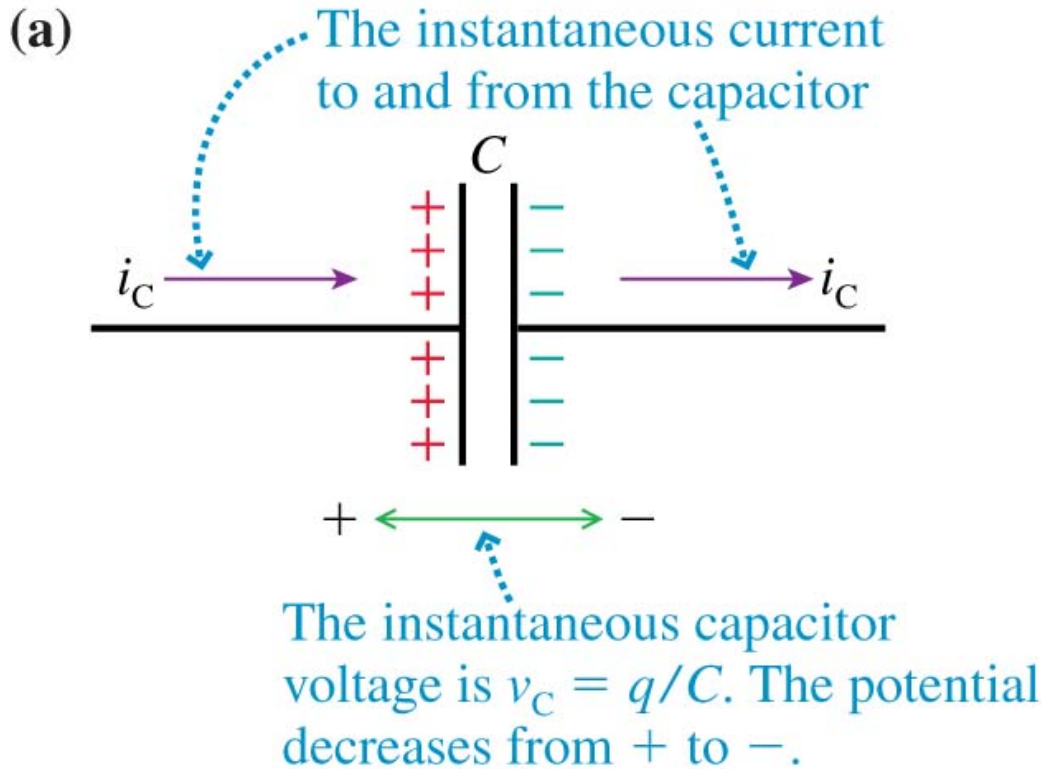


$$v_c = V_c \cos(\omega t)$$

$$q = Cv_c = CV_c \cos(\omega t)$$

$$i_c = \frac{dq}{dt} = -\omega CV_c \sin(\omega t)$$

$$i_c = \omega CV_c \cos\left(\omega t + \frac{\pi}{2}\right) \equiv$$
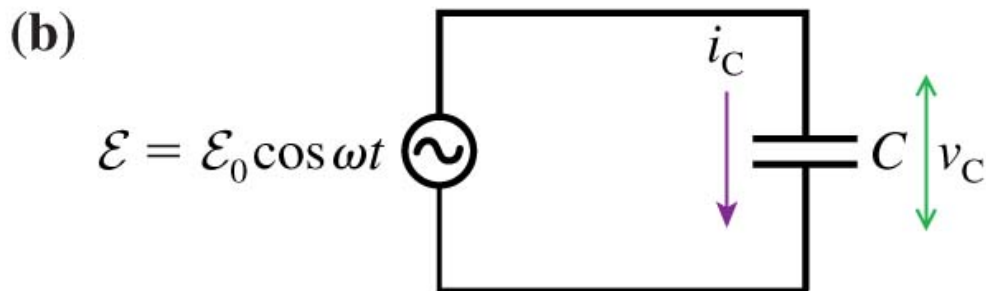
$$\equiv I_C \cos\left(\omega t + \frac{\pi}{2}\right)$$




$$v_c = V_c \cos(\omega t)$$


$$i_c = I_c \cos(\omega t + \frac{\pi}{2})$$

$$I_c \equiv \omega C V_c$$


**FIGURE 36.5** Graph and phasor diagram of the resistor current and voltage. The current and voltage are in phase.

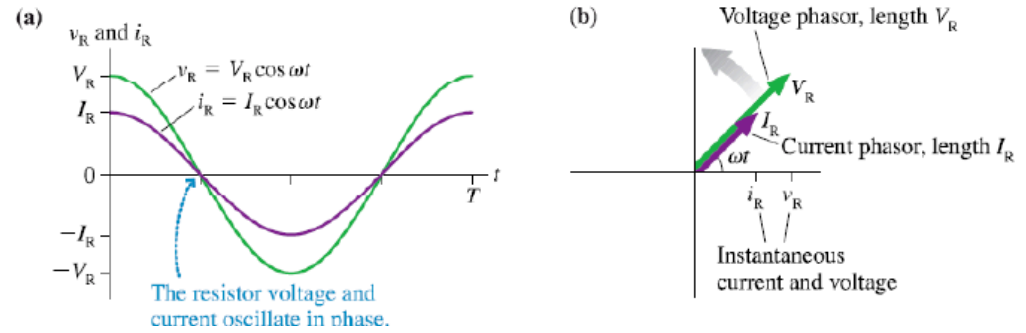

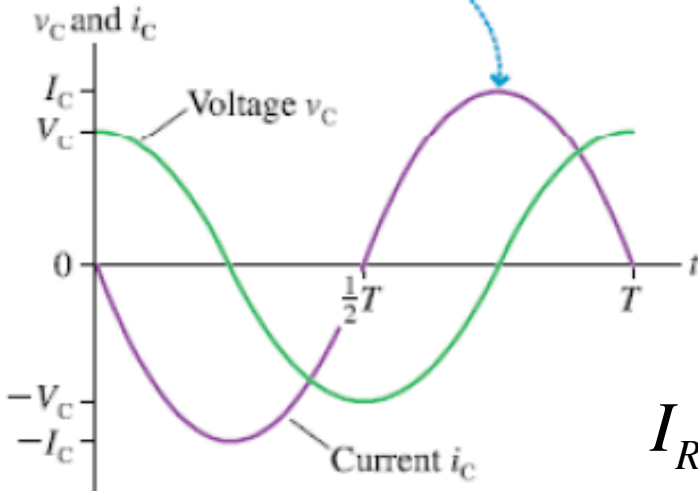(a)  $i_c$  peaks  $\frac{1}{4}T$  before  $v_c$  peaks. We say that the current *leads* the voltage by  $90^\circ$ .



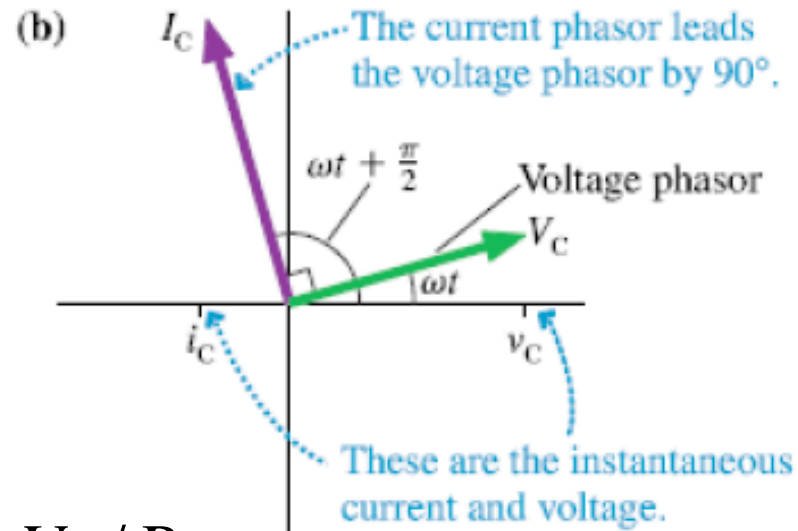Lead if in the cycle peak occurs first or is ahead in the phasor ccw rotation




$$I_R = V_R / R$$

$$I_C = V_c / X_C$$

$$X_C \equiv 1 / \omega C$$

Capacitive Reactance  
 - ohms

# AC Circuit: Capacitors

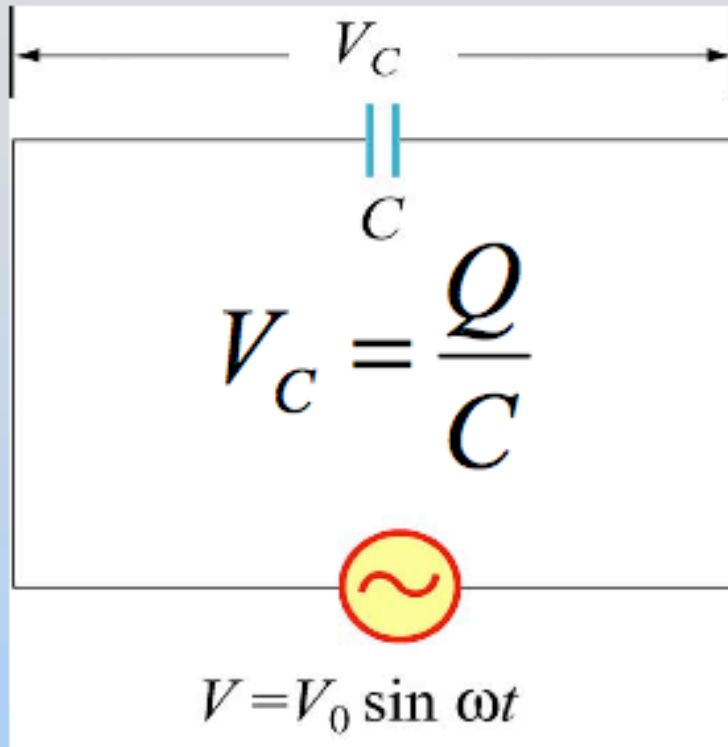

$$I_C(t) = \frac{dQ}{dt}$$


$$= \omega C V_0 \cos \omega t$$

$$= I_0 \sin(\omega t - \pi/2)$$

$$I_0 = \omega C V_0$$

$$\varphi = -\pi/2$$

$I_C$  leads  $V_C$  by  $\pi/2$


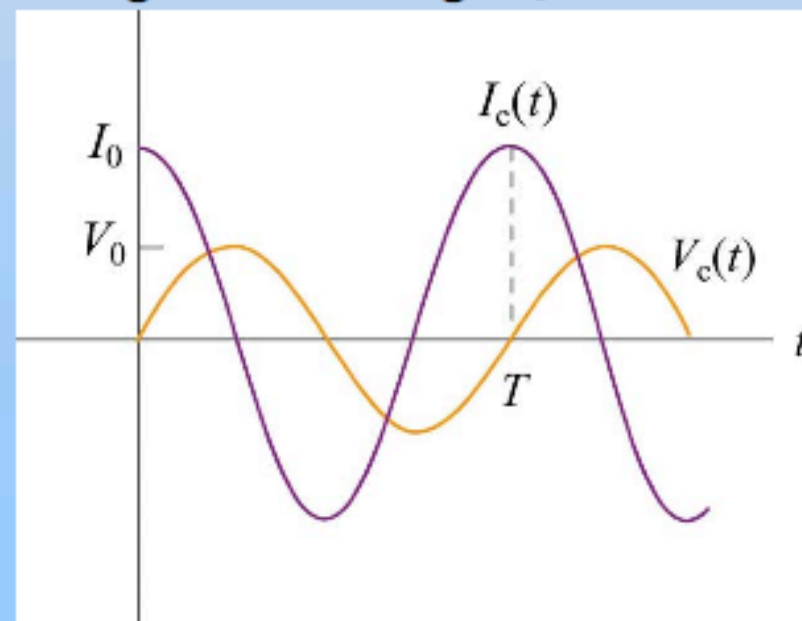


$$Q(t) = C V_C = C V_0 \sin \omega t$$

## AC Circuits - Capacitors

**ASSESS** Using reactance is just like using Ohm's law, but don't forget it applies to only the *peak* current and voltage, not the instantaneous values.

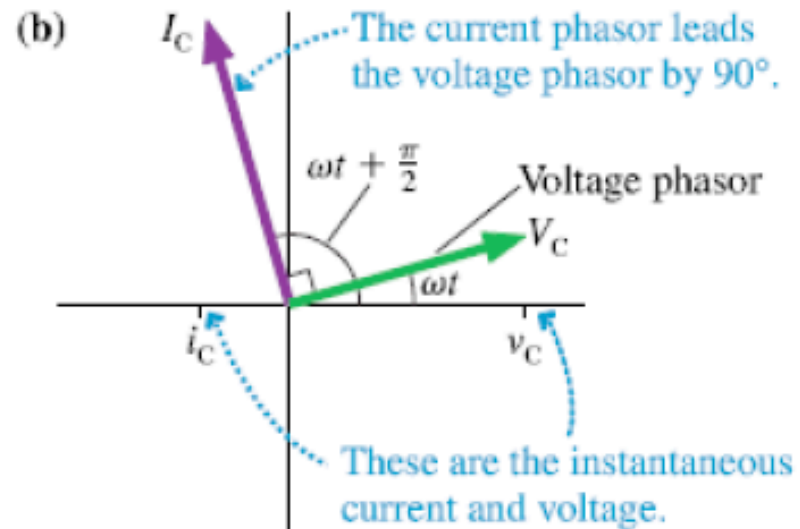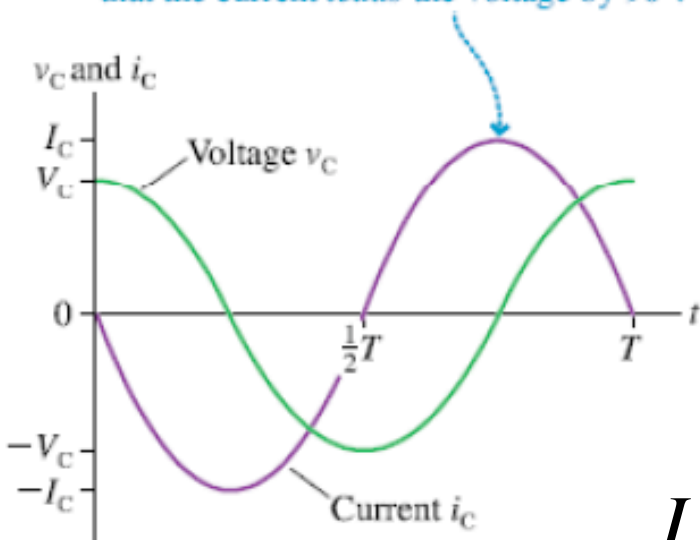- (a)  $i_C$  peaks  $\frac{1}{4}T$  before  $v_C$  peaks. We say that the current *leads* the voltage by  $90^\circ$ .



$$I_C = V_C / X_C$$

$$X_C = 1 / \omega C$$

# Capacitor Circuits

The instantaneous voltage across a single capacitor in a basic capacitor circuit is equal to the instantaneous emf:

$$v_C = V_C \cos \omega t$$

Where  $V_C$  is the maximum voltage across the capacitor, also equal to the maximum emf. The instantaneous current in the circuit is

$$i_C = \omega C V_C \cos \left( \omega t + \frac{\pi}{2} \right)$$

**The AC current to and from a capacitor *leads* the capacitor voltage by  $\pi/2$  rad, or  $90^\circ$ .**



**FIGURE 36.10** The capacitive reactance as a function of frequency.

